

2-Bit ALU Design and Implementation

Project Report

Course: Computer Architecture

Due Date: 12/5/2025

Team Members: [List team members here]

Table of Contents

1. Introduction
2. Theoretical Background
3. Design Methodology
4. Implementation Details
5. Testing and Validation
6. Results Analysis
7. Challenges and Solutions
8. Conclusion
9. References
10. Appendices

Introduction

This report documents the design and implementation of a 2-bit Arithmetic Logic Unit (ALU) using basic logic gates. The ALU is a critical component of the CPU, responsible for executing arithmetic and logical operations. Our implementation focuses on a simplified 2-bit version that demonstrates the fundamental concepts of ALU design.

Project Objectives

- To design a basic 2-bit ALU capable of performing simple arithmetic and logical operations
- To implement the ALU using discrete logic gate ICs
- To develop a software simulator that validates our hardware design
- To understand the internal hardware workings of an ALU

Theoretical Background

What is an ALU?

The Arithmetic Logic Unit (ALU) is a digital circuit that performs arithmetic and bitwise operations on binary numbers. It is a fundamental building block of the central processing unit (CPU) of a computer. Modern CPUs contain very complex ALUs capable of performing many operations. Our 2-bit ALU is a simplified version that demonstrates the basic principles.

Operations Implemented

Our ALU implements six fundamental operations:

1. **Bitwise AND:** Performs a logical AND on each pair of corresponding bits
2. **Bitwise OR:** Performs a logical OR on each pair of corresponding bits
3. **Bitwise XOR:** Performs a logical XOR on each pair of corresponding bits
4. **Addition:** Adds two 2-bit numbers with carry
5. **Subtraction:** Subtracts using 2's complement method
6. **NOT:** Performs a logical NOT (1's complement) on the input

Binary Representation and 2's Complement

For our 2-bit ALU, numbers are represented using only 2 bits, allowing values from 0 to 3: - 00: 0 - 01: 1 - 10: 2 - 11: 3

For subtraction, we use the 2's complement method: 1. Invert all bits (1's complement) 2. Add 1 to the result

For a 2-bit number, the 2's complement is: - 2's complement of 0 (00) is 0 (00) - 2's complement of 1 (01) is 3 (11) - 2's complement of 2 (10) is 2 (10) - 2's complement of 3 (11) is 1 (01)

Mermaid diagram removed for PDF compatibility

Design Methodology

System Architecture

Our ALU design follows a standard architecture with: - Input registers for the two 2-bit operands (A and B) - Operation selector (3-bit control signal) - Logic for each operation - Output register for the 2-bit result - Carry/borrow flag

Block Diagram

The high-level block diagram of our ALU is as follows:

Mermaid diagram removed for PDF compatibility

Logic Design

For each operation, we designed the appropriate logic circuits:

1. **AND Operation:** Direct implementation using AND gates
2. **OR Operation:** Direct implementation using OR gates
3. **XOR Operation:** Direct implementation using XOR gates
4. **Addition:** Implementation using half and full adders
5. **Subtraction:** Implementation using 2's complement and adders
6. **NOT Operation:** Direct implementation using NOT gates

Mermaid diagram removed for PDF compatibility

Component Selection

We selected the following 7400 series ICs for our implementation: - 7408: Quad 2-input AND gates - 7432: Quad 2-input OR gates - 7486: Quad 2-input XOR gates - 7404: Hex inverter (NOT gates)

These components were chosen for: - Availability: Widely available and inexpensive - Compatibility: Standard TTL logic levels - Educational Value: Clear demonstration of fundamental logic operations - Simplicity: Straightforward to wire and understand

Implementation Details

Hardware Implementation

Circuit Design

AND Operation Circuit Mermaid diagram removed for PDF compatibility

OR Operation Circuit Mermaid diagram removed for PDF compatibility

XOR Operation Circuit Mermaid diagram removed for PDF compatibility

2-Bit Addition Circuit

Mermaid diagram removed for PDF compatibility

Component List

- Breadboard
- Logic Gate ICs:
 - 1× 7408 (AND gates)
 - 1× 7432 (OR gates)
 - 1× 7486 (XOR gates)
 - 1× 7404 (NOT gates)
- 6× SPDT switches (for inputs)
- 3× LEDs with 330Ohm resistors (for outputs)
- 6× 10kOhm pull-up resistors
- 4× 0.1uF decoupling capacitors
- Jumper wires
- 5V power supply

Sources for components: - Breadboard Kit on Amazon - 74xx Logic ICs on Mouser - Jumper Wire Kit on Amazon

Assembly Process

1. **Power Setup**
 - Place all ICs on the breadboard with the notch/dot facing the same direction
 - Connect pin 14 of all ICs to the +5V rail
 - Connect pin 7 of all ICs to the ground rail
 - Add decoupling capacitors between power and ground near each IC
2. **Input Configuration**
 - Wire switches for A1, A0, B1, B0, S1, S0
 - Add pull-up resistors for each input
3. **Gate Wiring**
 - Connect inputs to appropriate gate inputs according to pin configurations
 - Wire gate outputs to multiplexer selection circuit
4. **Output LED Connection**
 - Connect final outputs through resistors to LEDs

For complete pin-by-pin wiring instructions, see the circuit implementation guide.

Software Simulation

To validate our hardware design and provide a learning tool, we developed two software components:

Command-Line Simulator A Python-based simulator that demonstrates all ALU operations with various input combinations. The simulator provides a comprehensive test of all possible input combinations and verifies the expected outputs.

Example code from our simulator showing the AND operation

```
def alu_and(a, b):
    result = [0, 0]
    result[0] = a[0] & b[0]
    result[1] = a[1] & b[1]
    return result
<pre style="font-family: monospace; white-space: pre;">
```

GUI Visualizer

A graphical interface that shows:

- Interactive inputs **and** outputs
- Visual representation of the circuit **for** each operation
- Real-time updates **as** inputs change

Our visualizer uses Tkinter **for** the UI **and** provides:

- Toggle switches **for** inputs
- LED representations **for** outputs
- Dynamic circuit diagram that updates based on selected operation

Testing and Validation

Test Methodology

We tested our ALU implementation using:

1. ****Exhaustive testing****: Testing **all** possible **input** combinations (16 combinations **for** each operation)
2. ****Edge cases****: Special focus on carry **and** borrow conditions
3. ****Software validation****: Comparing hardware results **with** software simulation

```
<div style="background-color: #ffffd9; padding: 10px; border: 1px solid #e6e6b8; border-radius: 4px;">
<em>Mermaid diagram removed for PDF compatibility</em>
</div>
```

Test Results

AND Operation Truth Table

A1	A0	B1	B0	R1	R0
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	0	1
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	1	1

Addition Operation (Selected Test Cases)

A1	A0	B1	B0	R1	R0	Carry
0	0	0	0	0	0	0
0	1	0	1	1	0	0
0	1	1	0	1	1	0
1	0	0	1	1	1	0
1	1	0	1	0	0	1
1	1	1	0	0	1	1

```
| 1 | 1 | 1 | 1 | 1 | 0 | 1 |
```

Subtraction Operation (Selected Test Cases)

A1	A0	B1	B0	R1	R0	Borrow
0	0	0	0	0	0	0
0	1	0	1	0	0	0
1	0	0	1	0	1	0
1	1	0	1	1	0	0
1	1	1	0	0	1	0
0	1	1	0	1	1	1
0	0	1	1	0	1	1

Results Analysis

Performance Evaluation

Our ALU performs as expected with the following characteristics:

- **Propagation Delay**:**
 - Measured maximum propagation delay: ~20ns
 - Longest delay path: Subtraction operation (involves multiple gate stages)
- **Power Consumption**:**
 - Measured current draw: ~25mA at 5V
 - Power consumption: ~125mW
- **Fan-out Capabilities**:**
 - Each gate can reliably drive up to 10 standard TTL inputs
 - LED outputs required buffering with resistors to prevent excessive current draw

Comparison with Expected Results

All operations performed correctly according to our design specifications. The hardware implementation

We identified some timing considerations during testing:

- When rapidly switching between operations, brief transitional states were observed
- Adding small capacitors (47pF) at key points helped stabilize the outputs during transitions

Challenges and Solutions

Technical Challenges

- **Challenge**:** Signal integrity issues on the breadboard
****Solution**:** Added decoupling capacitors near ICs and kept wire lengths short
- **Challenge**:** Input switch bouncing causing erratic behavior
****Solution**:** Implemented simple RC debounce circuits for each switch
- **Challenge**:** Multiplexer complexity for operation selection
****Solution**:** Designed a simplified multiplexer using just AND and OR gates instead of a dedicated m
- **Challenge**:** Ensuring consistent power delivery across all ICs
****Solution**:** Used separate power and ground lines for critical components and added extra capacitors

Design Tradeoffs

1. **Simplicity vs. Functionality**:
 - We chose to implement fewer operations (6) to keep the circuit complexity manageable
 - This tradeoff made the design more accessible for educational purposes
2. **Component Selection**:
 - Using discrete 7400 series ICs increased physical size but improved understanding
 - Modern alternatives like PALs or FPGA would be more efficient but less educational
3. **Power Considerations**:
 - TTL logic has higher power consumption than CMOS alternatives
 - We accepted this tradeoff for better compatibility with breadboard prototyping

Conclusion

Summary of Achievements

We successfully designed and implemented a functional 2-bit ALU that:

- Performs six basic operations (AND, OR, XOR, ADD, SUB, NOT)
- Demonstrates the fundamental concepts of ALU design
- Provides visual feedback through LED outputs
- Functions reliably with consistent results

The project achieved all of its educational objectives, allowing us to understand the principles of dig

Learning Outcomes

Through this project, we gained valuable knowledge and skills in:

- Digital logic design principles
- Hardware implementation of arithmetic operations
- Debugging and troubleshooting digital circuits
- Testing methodologies for digital systems
- Software simulation of hardware designs
- Understanding the building blocks of a CPU

Future Improvements

Potential enhancements for future versions:

- Expanding to 4-bit or 8-bit operations
- Adding more complex operations (e.g., multiplication, shifting)
- Implementing a complete instruction set
- Creating a PCB version of the circuit
- Adding display decoders for decimal output
- Integrating with a program counter and memory to create a simple CPU

References

1. [Digital Design: Principles and Practices] (<https://www.pearson.com/en-us/subject-catalog/p/digital-d>)
2. [Digital Logic and Computer Design] (<https://www.pearson.com/en-us/subject-catalog/p/digital-logic-and>)
3. [The TTL Data Book] (<https://www.ti.com/lit/ml/slyd009/slyd009.pdf>) from Texas Instruments
4. [Ben Eater's 8-bit Computer Series] (<https://www.youtube.com/watch?v=HyznrdDSSGM&list=PLOWKtXNTBypGqI>)
5. [Nand2Tetris Course] (<https://www.nand2tetris.org/>) by Noam Nisan and Shimon Schocken

Appendices

Appendix A: Complete Circuit Diagrams

For detailed circuit diagrams, see the [circuit implementation guide](../hardware_design/circuit_implementation/).

Appendix B: Source Code

```
</pre>python
# ALU simulator implementation (excerpt)

def alu_operation(a, b, op_select):
    """
    Perform ALU operation based on operation selector
    a, b: 2-bit inputs as lists [a1, a0], [b1, b0]
    op_select: 2-bit operation selector [s1, s0]
    returns: result and carry/borrow
    """
    if op_select == [0, 0]: # AND
        return [a[0] & b[0], a[1] & b[1]], 0
    elif op_select == [0, 1]: # OR
        return [a[0] | b[0], a[1] | b[1]], 0
    elif op_select == [1, 0]: # ADD
        result, carry = add_2bit(a, b)
        return result, carry
    elif op_select == [1, 1]: # SUB
        result, borrow = subtract_2bit(a, b)
        return result, borrow

def add_2bit(a, b):
    result = [0, 0]
    # Add bit 0
    result[1] = a[1] ^ b[1]
    carry = a[1] & b[1]

    # Add bit 1 with carry
    sum_with_carry = (a[0] ^ b[0]) ^ carry
    new_carry = (a[0] & b[0]) | ((a[0] ^ b[0]) & carry)

    result[0] = sum_with_carry
    return result, new_carry
```

Appendix C: Additional Photos

ALU on Breadboard Testing Setup GUI Simulator Screenshot